
Clocking Issues: Distribution, Energy

Prof. Dejan Marković

ee216a@gmail.com


UCLA

Clock Distribution

- ♦ **Goals:**
 - Deliver clock to all memory elements with acceptable skew
 - Deliver clock edges with acceptable sharpness
- ♦ **Clock network design is another one of the big challenges in the design of a large chip**
- ♦ **Clocks are generally distributed via wiring trees**
- ♦ **Want to use low-resistance interconnect to minimize delay**
- ♦ **Use multiple drivers to distribute driver requirements**
 - Use optimal sizing principles to design buffers
 - Clock lines can create significant crosstalk

Issues in Clock Distribution Network


 
- ◆ **Skew**
 - Process, voltage, temp.
 - Data dependence
 - Noise coupling
 - Load balancing
- ◆ **Power, CV^2f – (no $\frac{1}{2}$ or α)**
 - Clock gating
- ◆ **Flexibility/Tunability**
 - Compactness
 - fit into existing layout/design
- ◆ **Reliability**
 - Electromigration



See videos from P. Restle (IBM) on classwiki

Clock Distribution Methods


- | | |
|--|--|
| <ul style="list-style-type: none"> ◆ RC-Tree <ul style="list-style-type: none"> – Less capacitance – More accuracy – Flexible wiring | <ul style="list-style-type: none"> ◆ Grids <ul style="list-style-type: none"> – Reliable – Less data dependency – Tunable (late in design) |
|--|--|

  


Shown here for final stage drivers driving F-F loads

RC Trees, Clock Distribution

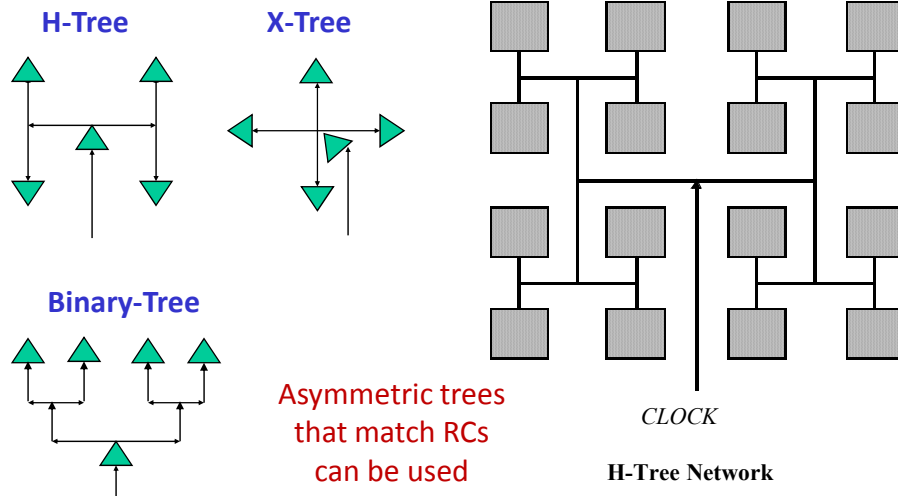- ◆ Observe: only relative skew is important




More Realistic H-Tree

 


[Restle98]

The Grid System

- ◆ No RC-matching
- ◆ Large power

 

DEC Alpha Examples

 


Examples of Distribution

H-Tree


Asymmetric RC-Tree

— IBM

 

Grids


DEC [Alphas]

 

Serpentines


Intel x86

[Young ISSCC97]

 


Examples of Processor Chips

**DEC-Alpha
21064 clock
spines**


 


Note: reverse Z-axis

 



**DEC-Alpha
21064 RC
delays**

  **DEC-Alpha
21164 RC delays
for *global*
distribution
Spine + Grid**




**DEC-Alpha
21164
RC *local*
delays**

  Example: EV5 (Alpha 21164) Clocking (1995)




 - ◆ Single-phase clocking
- ◆ 2 distributed driver channels
 - Reduced RC delay/skew
 - Improved thermal distribution
 - 3.75 nF clock load
 - 58 cm final driver width
- ◆ Local inverters for latching
- ◆ Conditional clocks in caches to reduce power
- ◆ More complex race checking
- ◆ Device variation




Example: EV6 (Alpha 21264) Clocking (1998)

600MHz, 0.35 μ m CMOS

 


Global clock waveform

 


- ◆ Multiple conditional buffered clocks
 - 2.8 nF clock load
 - 40 cm final driver width
- ◆ Reduced load/skew
- ◆ Reduced thermal issues
- ◆ Multiple clocks complicate race checking

21264 Clocking

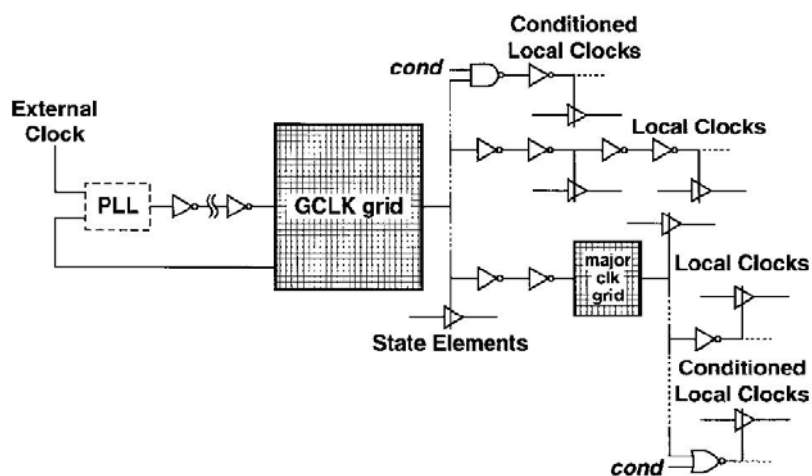


EV6 Clock Results

 

EV7 Clock Hierarchy, 2002

152 million transistors, 15/137 logic/memory

 Active Skew Management and Multiple Clock Domains



- ◆ Widely dispersed drivers
- ◆ DLLs compensate static and low-frequency variation
- ◆ Divides design and verification effort
- ◆ DLL design and verification is added work
- ◆ Tailored clocks

Alpha Processors Case Study


- ♦ **EV4 (21064) 0.75μm, 200 MHz ~ 1992**
 - Single global clock driver, 5 levels of buffering
 - 35 cm driver, 3.25 nF, 40% power
- ♦ **EV5 (21164) 0.5μm, 300 MHz ~ 1995**
 - One central, two side clock drivers
 - 58 cm driver, 3.75 nF, 40% power
- ♦ **EV6 (21264) 0.35μm, 600 MHz ~ 1998**
 - Clock grid, 4 window panes, hierarchical, gated clock domains
 - 40 cm driver, 2.8 nF
- ♦ **EV7 0.18μm, 1.2 GHz ~ 2002**
 - Multiple clock domains, DLLs

Intel Processors

	Pentium® II	Pentium® III	Pentium® 4
MPR Issue	June 1997	April 2000	Dec 2001
Clock Speed	266 MHz	1GHz	2GHz
Pipeline Stages	12/14	12/14	22/24
Transistors	7.5M	24M	42M
Cache (I/D/L2)	16k/16K/-	16K/16K/256K	12K/8K/256K
Die Size	203mm ²	106mm ²	217mm ²
IC Process	0.25μm, 4M	0.18μm, 6M	0.18μm, 6M
Max Power	27W	23W	67W


- ♦ **Increasing clock speeds and die size**
 - Balancing skew using simple RC trees becoming less effective
- ♦ **Insertion delay 7-8FO4 due to increased die**
 - Clock skew control harder to due to increasing PVT variations
- ♦ **Use of active deskewing circuits**

IA-32 Pentium Pro: Active Deskewing

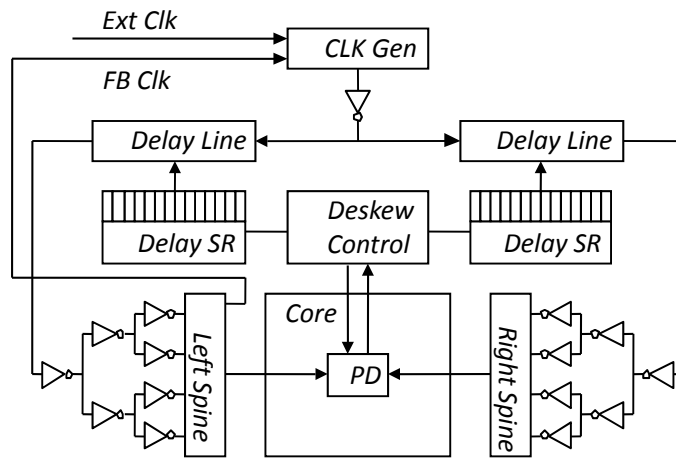


*Clock distribution network with deskewing circuit
[Geannopoulos and Dai 1998]*

IA-32 Pentium Pro: Delay Shift Register

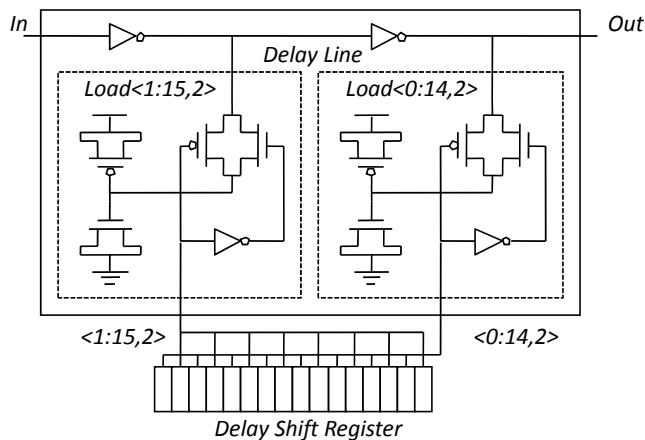


*Delay shift register
[Geannopoulos and Dai 1998]*

IA-32 Pentium Pro: Phase Detector

 

Phase detector
[Geannopoulos and Dai 1998]

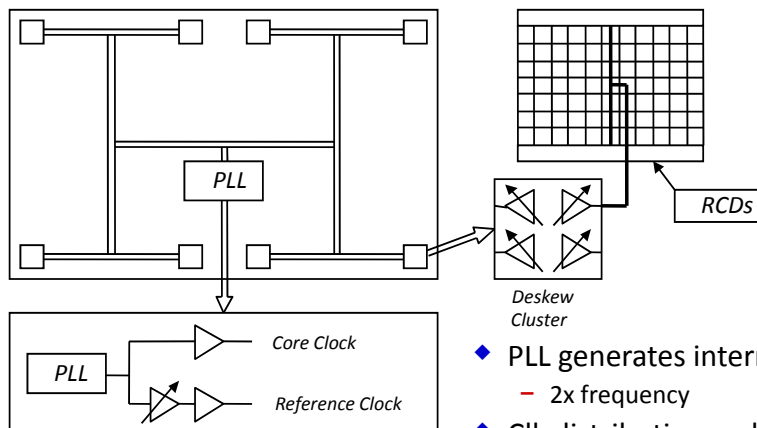First IA-64 Processor: Clock Distribution




Clock distribution topology
[Rusu and Tam 2000]

- ◆ PLL generates internal clock
 - 2x frequency
- ◆ Clk distribution architecture
 - Balanced global clock tree
 - Multiple deskew buffers
 - Multiple local clock buffers

Result of Active Deskewing

♦ Measured regional clock skew

 

[Rusu and Tam 2000]

Some Energy Reduction Ideas

♦ Clock gating

- Global
- Local

♦ Low-swing clocking


- Reduced-swing Clk drivers
- CSE redesign
- N-only CSE w/ low-swing Clk

♦ Dual-edge triggering

- Latch-mux
- Pulsed-latch

Global Clock Gating

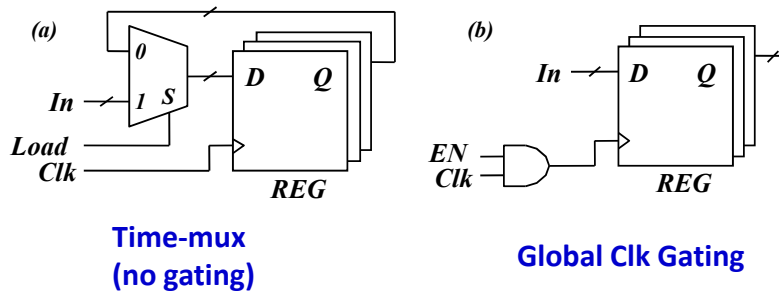
- ♦ Used to save clocking energy when data activity is low



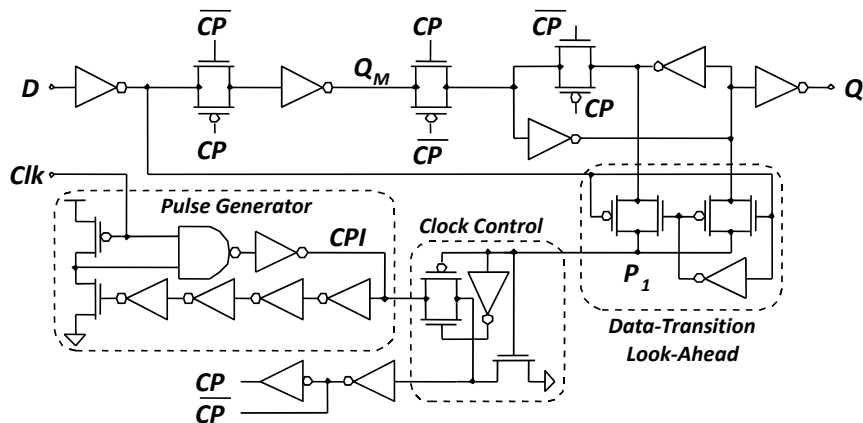(a) Nongated clock circuit, (b) gated clock circuit.
[Kitahara et al. 1998]

Local Clock Gating (Requires FF Redesign)


- ♦ Same concept, control at a fine level of granularity (single FF)



Data-transition look-ahead latch
[Nogawa and Ohtomo, 1998]

Local Clock Gating, Another Example


- ◆ Clock enabled only when $D \neq Q$

 

Conditional-capture FF
[Kong et al. 2000]

Gated Transmission-Gate M-S Latch

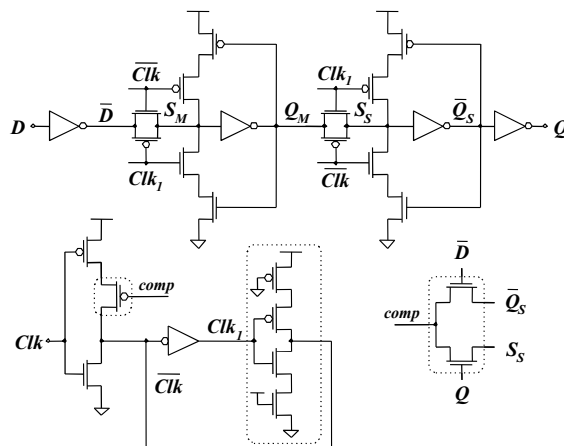
- ◆ Concept:
inhibit clock when
 $D = Q$
 - $comp = D \text{ XNOR } Q$
 - $comp = 0$ ($D \neq Q$),
M-S Latch
 - **$comp = 1$ ($D = Q$),**
 $\overline{Clk} = 0, Clk_1 = 1 \Rightarrow$
latches closed, no
output change, no
internal power




Gated M-S latch
[Markovic et al. 2001]

Gated TG MS Latch: Timing and Energy

Setup (U) and Hold time (H)

 


Energy

 

- ◆ Increased t_{setup} in gated MSL due to inclusion of the comparator into the critical path \Rightarrow slower than conventional MSL
- ◆ Smaller energy per transition if switching activity of D is < 0.3
 - For higher α , comparator and Clk gen dominate the energy


Data-Transition Look-Ahead (DTLA) Pulsed Latch

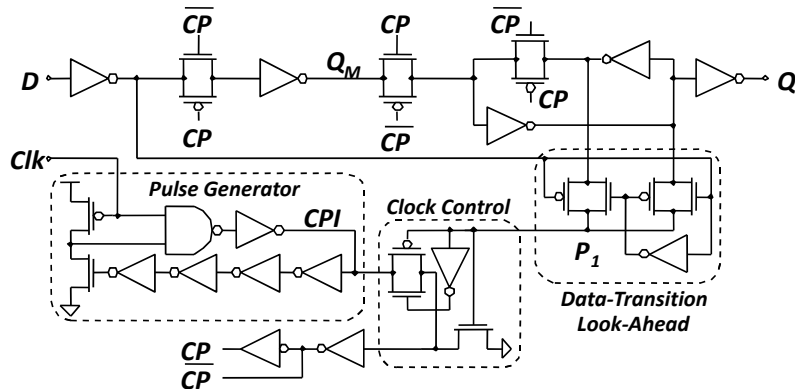- ◆ Pulsed latch, Clk pulses are gated with XOR DTLA circuit
 - If $D \neq Q \Rightarrow P_1 = 0$, circuit operates as a conventional pulsed-latch
 - If $D = Q \Rightarrow P_1 = 1 \Rightarrow CP = 0$, no Q change or energy consumption
- ◆ XOR and Clk Control in the critical path \rightarrow large t_{setup} , and t_{D-Q}




[Nogawa and Ohtomo, 1998]

DTLA-L: Analysis of Energy Consumption

 

DTLA-L without clock gating

 

DTLA-L Pulse Generator

$$E_{CMSL} = \frac{\alpha}{2} \cdot (E_{0-1} + E_{1-0}) + \frac{1-\alpha}{2} \cdot E_{Clk} + E_{Cin}$$

$$E_{DL-DFF} = \frac{\alpha}{2} \cdot (E_{0-1} + E_{1-0}) + \frac{1-\alpha}{2} \cdot E_{D-idle}$$

$$E_{0-1} = E_{D-idle} + E_{CLK} + E_{DL+CC} + E_{int} + E_{ext}$$


$$E_{1-0} = E_{D-idle} + E_{CLK} + E_G + E_{int}$$

$$E_{D-idle} = E_{0-0} = E_{1-1} = \frac{E_{PG}}{N} + E_{Cin}$$


PG shared among N DTLA-L's
 α – input switching activity

Energy Comparison: DTLA-L vs. Conventional M-S

 - DTLA-L is more energy-efficient than CMSL when $N > 2$ and $\alpha < 0.25$



$E(\text{DTLA-L}) < E(\text{CMSL})$

 


$E(\text{DTLA-L}) > E(\text{CMSL})$

Clock-on-Demand (COD) Pulsed-Latch


- ◆ Pulsed latch, Clk pulses gated with XNOR DTLA ckt

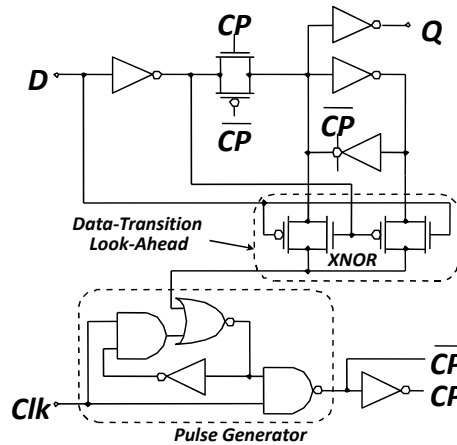- If $D \neq Q \Rightarrow \text{XNOR}=0$, $\text{CP} \rightarrow 1$ when $\text{Clk} \uparrow$, and $\text{CP} \rightarrow 0$ after Q has changed to D
- If $D=Q \Rightarrow \text{XNOR}=1 \Rightarrow \text{CP}=0$, no Q change or energy consumption




[Hamada et al., 1999]

 Energy-Efficient Pulse Generator in COD-PL



- ◆ Straightforward realization with CMOS gates

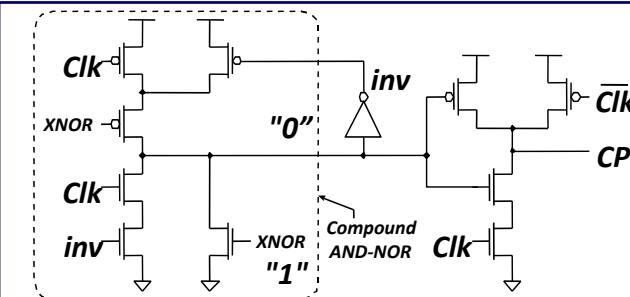- C_{int} switches in each cycle
- Energy-inefficient




- ◆ Compound AND-NOR gate

- Energy-efficient

Circuit Sizing Impacts Energy Efficiency of COD-PL

 
- ◆ COD-PL more effective for high-speed due to large Clk transistors



[Markovic et al., 2001]


Conditional-Capture Flip-Flop (CCFF)

 - ◆ First stage: pulse generator with internal clock gating
 - When $\text{Clk}=1$, $\bar{S}=\bar{R}=1$
 - When $\text{Clk}=1$, $\text{Clk}_1=0$, S can switch low if $D=1$, \bar{Q} can switch low if $D=0$, $Q=1$
 - Otherwise, $\bar{S}=\bar{R}=1 \rightarrow$ no energy consumed
- ◆ Second stage: pass-gate implementation of SAFF
- ◆ No t_{setup} degradation due to clock gating



[Kong et al. 2000]

Timing Comparison

 

Designs with Clk gating / Delay:

- ◆ Relative delay constant w/ V_{DD}
- ◆ Large delay due to long t_{setup}


Internal race immunity:

- ◆ $R(\text{FF}) < R(\text{MSL}) < R(\text{Gated MSL})$
- ◆ COD-PL bad (wide Clk pulse)

[Markovic et al. 2001]

Low-Swing Clocking: Driver Re-design

 
- ◆ Half-swing clock drivers: 50% power reduction (minus some penalty in clock drivers)



[Kojima et al. 1995]

N-only Clocked Latches

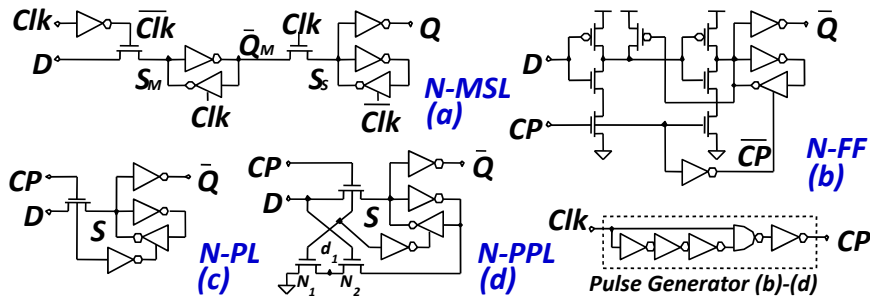- Bring clock only to n-MOS transistors to allow reduced clock swing without conflict with partially turned-off p-MOS transistors
- Reduced clocking energy with some penalty in performance
 - Clk is in the critical path



(a) conventional TG MSL, (b) pulsed-latch, (c) conventional PL, (d) push-pull PL

Low-Clk-Swing FFs: Energy-Delay Comparison


Full-swing:

- PL preferred for high-speed
- MSL preferred for low energy

Low-swing clock:

- N-FF preferred for high-speed
- N-PPL is preferred for low energy

 
130nm technology,
 $C_L = 50\text{fF}$, $C_{in} \leq 12.5\text{fF}$,
 $\alpha = 0.1$



[Markovic et al. 2004]


Effect of Clock Noise on Latch Delay

 - All latches fail for clock noise > 12% of clock voltage
- N-FF gives best clock noise rejection




Dual-Edge Triggering: Latch-Mux

 - ◆ Saves clocking energy *regardless* of data activity!
- ◆ Extra Mux → longer delay




DET Latch-Mux: Circuit Example

 - ♦ **Pass-gate latches**
 - One transparent when $Clk = 0$
 - One transparent when $Clk = 1$
- ♦ **Pass-gate multiplexer that selects the output of the opaque latch**



C²MOS Latch-Mux (C²MOS-LM)

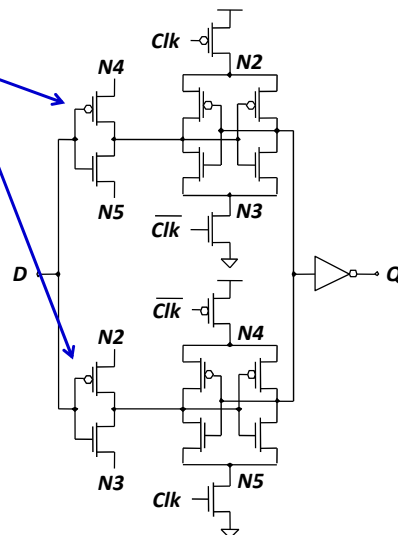
- ♦ **C²MOS latches**
 - One transparent when $Clk = 1$
 - One transparent when $Clk = 0$
- ♦ **Multiplexer: two C²MOS inverters that propagate the output of the opaque latch**
- ♦ **Large clock transistors shared between the latches and the multiplexer**




[Gago et al., 1993]

Dual-Edge Triggering: Pulsed-Latch

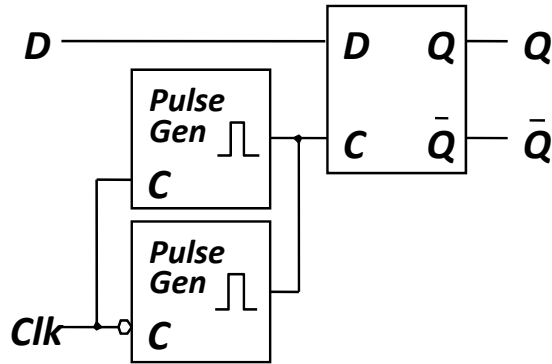- ◆ First stage: pulse generator
- ◆ Second stage: capturing latch




DET Pulsed-Latch Circuit Example

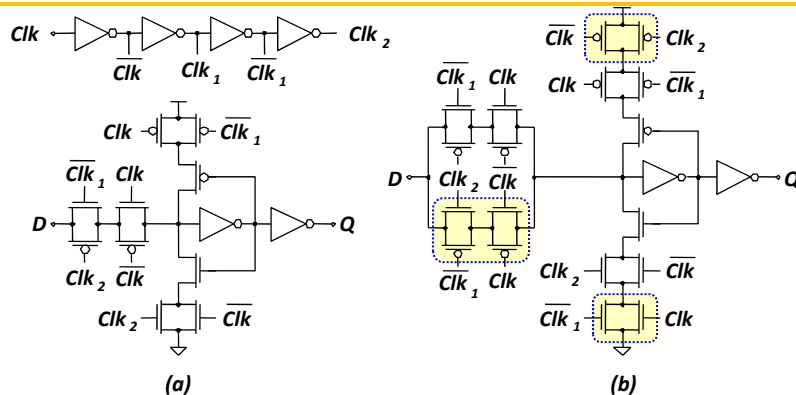

- ◆ Pulse generator transparent to D only when $Clk = \overline{Clk}_1 = 1$, or when $Clk = \overline{Clk}_2 = 1 \Rightarrow$ shortly after both edges of the clock
- ◆ DET PL consumes lot of energy for four clocked pass gates
- ◆ To improve speed, modified from original design (*Strollo et al., 1999*) which implemented n-MOS pass gate and p-MOS keeper

Dual-Edge Triggered Flip-Flop

- ◆ Based on SR latch

 


DET Flip-Flop Circuit Example

- ◆ Two pulse generators:
X active at rising edge of the clock, Y active at falling edge of the Clk


- ◆ S_X and S_Y alternately precharge / evaluate

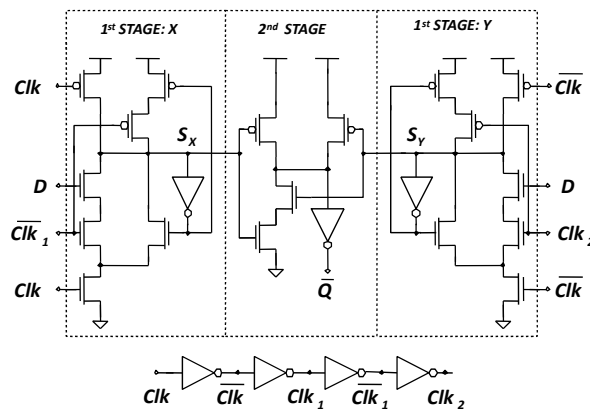- At any moment, one of S_X and S_Y keeps the value of data sampled at the most recent clock edge
- The other S_X or S_Y is precharged high



- ◆ Pulses at S_X and S_Y have same width as clock
- ◆ Second stage is a simple NAND gate \Rightarrow no need for a latch


SET vs. DET: Delay Comparison

 

- ◆ Latch-MUX's have two equally critical paths, somewhat shorter than that of MSL
- ◆ PL is more complex, adding more capacitance to the critical path compared to SET PL
- ◆ SPGFF has short domino-like critical path \Rightarrow fastest


SET vs. DET: Power Consumption

 - ◆ LM's benefit from clever implementation of latch-mux structure with clock transistors sharing
- ◆ PL adds extra high-activity capacitance compared to SET PL
- ◆ SPGFF power consumption is in the middle, mainly due to alternate switching of nodes SX and SY



(0.18 μm , 500MHz for SET,
250MHz for DET, high load)


SET vs. DET: EDP Comparison

 


- ◆ Latch-MUX's have similar or better EDP than their SET peers
- ◆ PL exhibits worse delay and energy compared to SET PL, due to more complex design
- ◆ SPGFF is fastest with moderate energy consumption: lowest EDP
- ◆ $EDP (SPGFF) < EDP (LM) < EDP (PL)$

Clock Distribution for DET

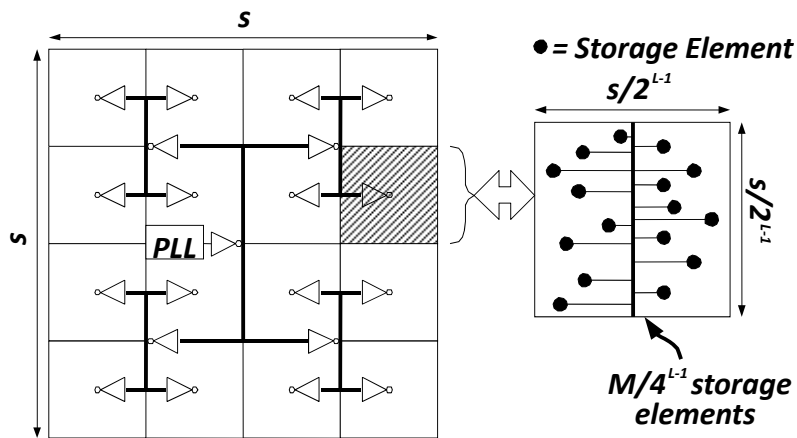- ◆ H-tree clock distribution with L levels of clock buffers
 - Example below: $L = 3$



SET vs. DET: Clocking Power

 

- ♦ DET wins if the total clock load capacitance is $< 2x$ the capacitance of a SET design